

# Chapter 31 Electromagnetic Oscillations and Alternating Current

## LC Oscillations, Qualitatively

● In the  $LC$  circuit the charge, current, and potential difference vary sinusoidally (with period  $T$  and angular frequency  $\omega$ ). The resulting oscillations of the capacitor's electric field and the inductor's magnetic field are said to be **electromagnetic oscillations**.


● The energy stored in the electric field of the capacitor is  $U_E = \frac{q^2}{2C}$


● The energy stored in the magnetic field of the inductor is  $U_B = \frac{Li^2}{2}$

● To determine the charge  $q(t)$  on the capacitor, put in a voltmeter to measure the potential difference (or *voltage*)  $v_C$  that exists across the capacitor  $C$ :  $v_C = \frac{q}{C}$

● To measure the current, connect a small resistance  $R$  in series in the circuit and measure the potential difference  $v_R$  across it:

$$v_R = iR$$

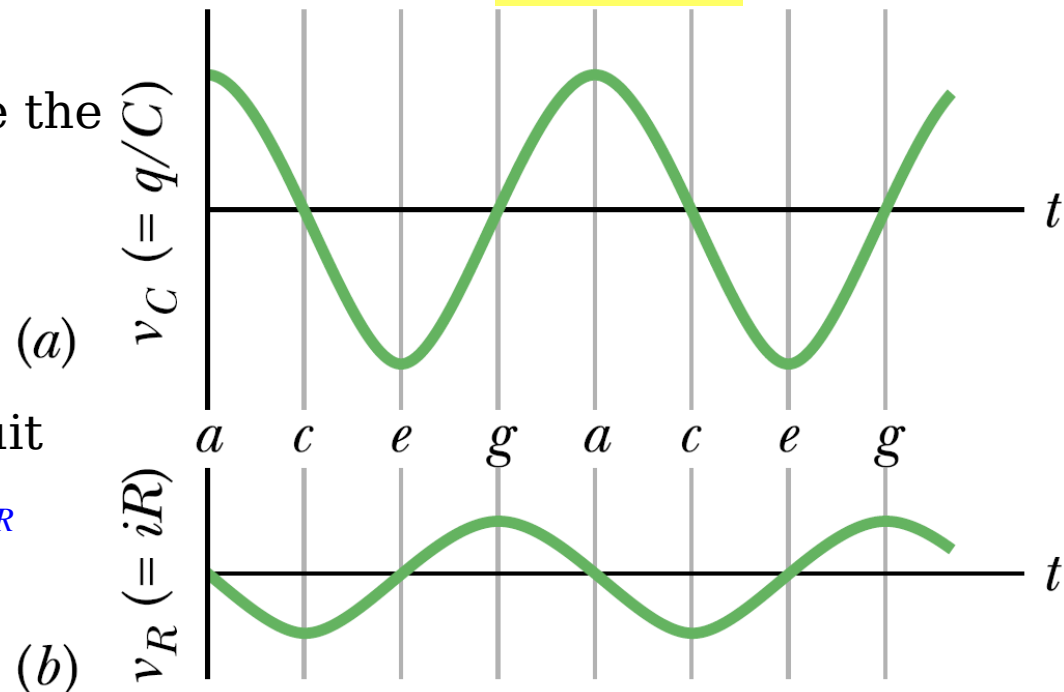

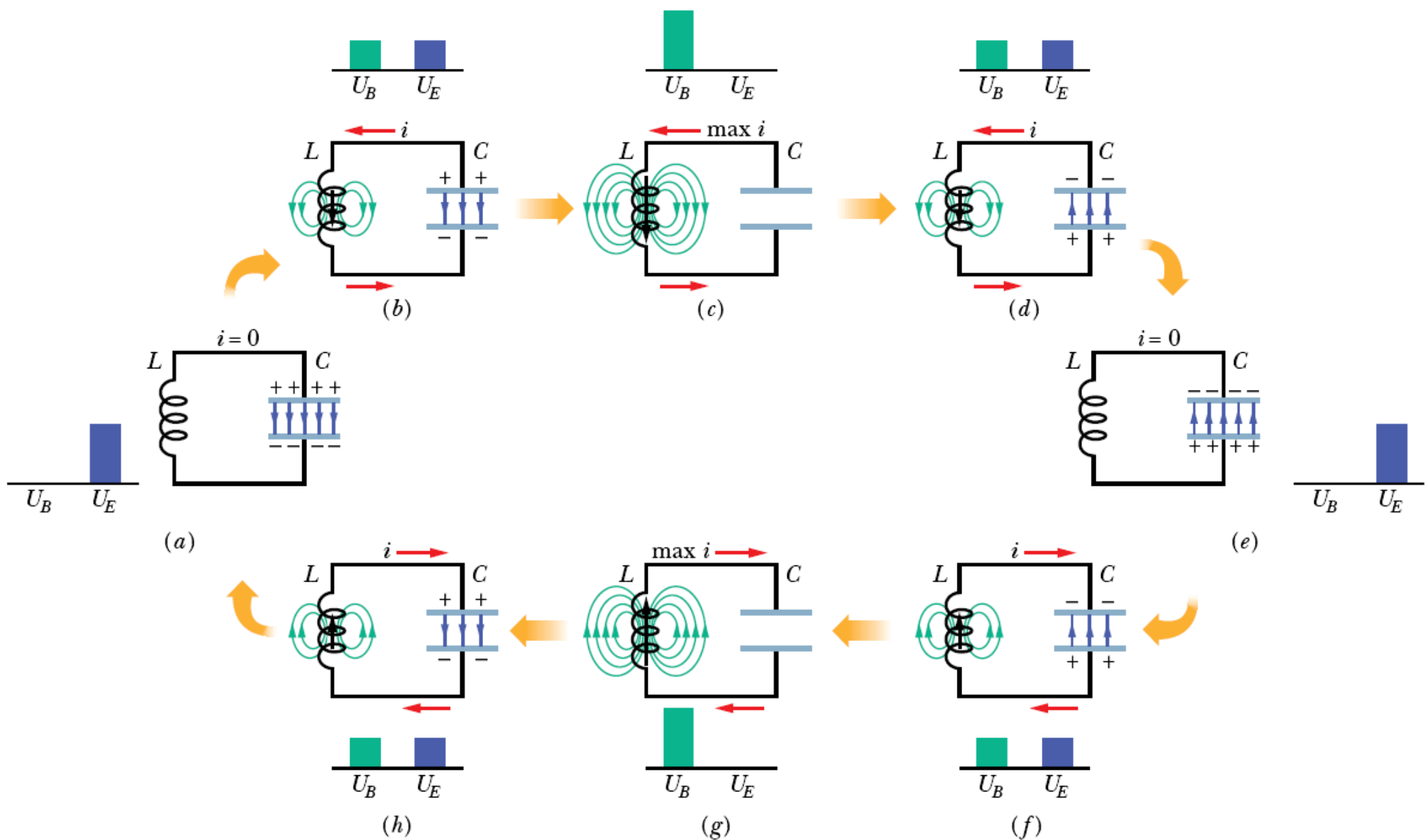

● In an actual  $LC$  circuit, the oscillations will not continue indefinitely because there is always some resistance present that will drain energy from the electric and magnetic fields and dissipate it as thermal energy (the circuit may become warmer).

# The Electrical- Mechanical Analogy


- The analogy between the oscillating  $LC$  system and an oscillating block-spring system:

$q$  corresponds to  $x$ ,  $1/C$  correspond to  $k$   
 $i$  corresponds to  $v$ ,  $L$  correspond to  $m$

- These correspondences suggest that in an  $LC$  oscillator, the capacitor is mathematically like the spring in a block-spring system and the inductor is like the block.

- In a block-spring system:  $\omega = \sqrt{\frac{k}{m}}$

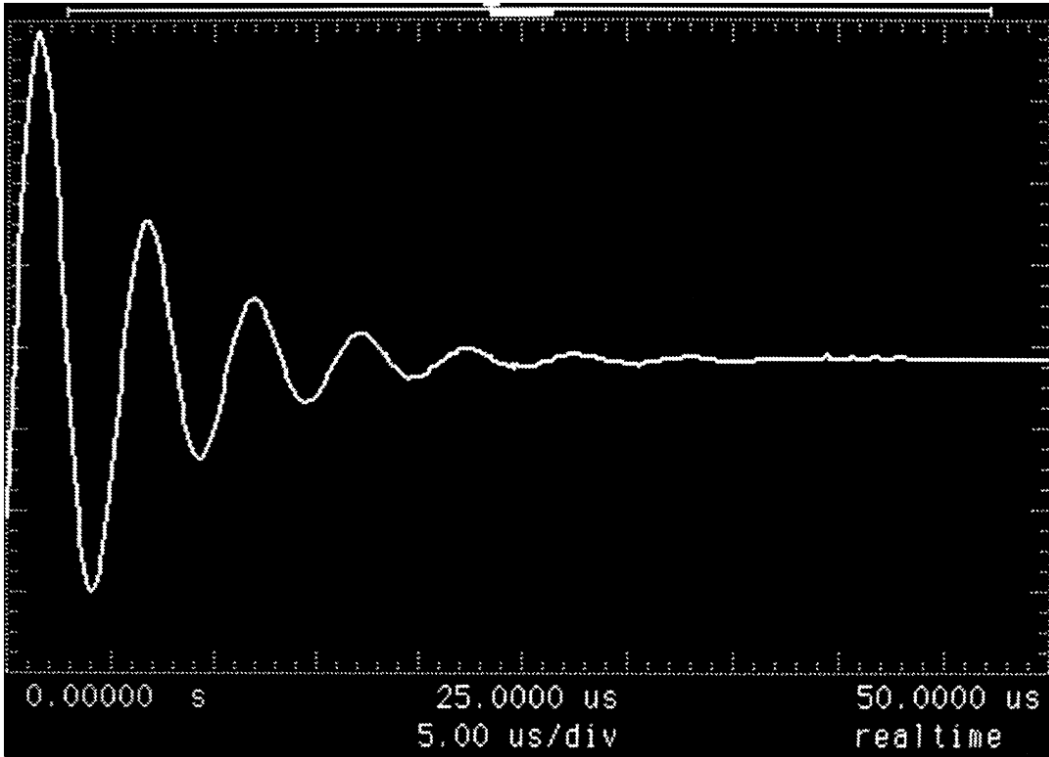- The correspondences suggest that to find the angular frequency of oscillation for an ideal  $LC$  circuit,  $k$  should be replaced by  $1/C$  and  $m$  by  $L$ ,



$$\omega = \frac{1}{\sqrt{LC}} \quad LC \text{ circuit}$$

Block-Spring System		$LC$ Oscillator	
Element	Energy	Element	Energy
Spring	Potential, $k x^2/2$	Capacitor	Electrical, $q^2/2 C$
Block	Kinetic, $m v^2/2$	Inductor	Magnetic, $L i^2/2$
	$v = d x / d t$		$i = d q / d t$

## LC Oscillations, Quantitatively

### The Block-Spring Oscillator

● The total energy of a block-spring oscillator:  $U = U_b + U_s = \frac{1}{2} m v^2 + \frac{1}{2} k x^2$

● Energy conservation, no friction:

$$0 \leftarrow \frac{dU}{dt} = \frac{d}{dt} \left( \frac{1}{2} m v^2 + \frac{1}{2} k x^2 \right) = m v \frac{dv}{dt} + k x \frac{dx}{dt} \Rightarrow m \frac{d^2 x}{dt^2} + k x = 0$$

$$\Rightarrow x(t) = X \cos(\omega t + \phi) \quad \text{displacement}$$

$X$  is the amplitude of the mechanical oscillations,  $\omega$  is the angular frequency of the oscillations, and  $\phi$  is a phase constant.

### The LC Oscillator

● The total energy in an oscillating LC circuit:  $U = U_B + U_E = \frac{1}{2} L i^2 + \frac{1}{2} \frac{q^2}{C}$

$U_B$  is the energy stored in the magnetic field of the inductor and  $U_E$  is the energy stored in the electric field of the capacitor.

● Energy conservation, no resistance:

$$0 \leftarrow \frac{dU}{dt} = \frac{d}{dt} \left( \frac{1}{2} L i^2 + \frac{1}{2} \frac{q^2}{C} \right) = L i \frac{di}{dt} + \frac{q}{C} \frac{dq}{dt} \Rightarrow L \frac{d^2 q}{dt^2} + \frac{1}{C} q = 0 \quad \text{LC oscillation}$$

$$\Rightarrow q(t) = Q \cos(\omega t + \phi) \quad \text{charge}$$

- The current of the  $LC$  oscillator:

$$i(t) = \frac{dq}{dt} = -\omega Q \sin(\omega t + \phi) = -I \sin(\omega t + \phi) \quad \text{current} \quad \Leftarrow \quad I = \omega Q$$

- The angular frequency of the  $LC$  oscillator:

$$\frac{d^2 q}{dt^2} = -\omega^2 Q \cos(\omega t + \phi) \Rightarrow -L \omega^2 Q \cos(\omega t + \phi) + \frac{Q}{C} \cos(\omega t + \phi) = 0$$

$$\text{since } L \frac{d^2 q}{dt^2} + \frac{q}{C} = 0 \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

- $\phi$  is determined by the initial conditions.

- The electrical energy stored in the  $LC$  circuit

$$U_E = \frac{q^2}{2C} = \frac{Q^2}{2C} \cos^2(\omega t + \phi)$$


- The magnetic energy stored in the  $LC$  circuit

$$U_B = \frac{Q^2}{2C} \sin^2(\omega t + \phi) \quad \Leftarrow \quad U_B = \frac{L i^2}{2} = \frac{L \omega^2 Q^2}{2} \sin^2(\omega t + \phi)$$

Note: (1)  $(U_E)_{\max} = (U_B)_{\max} = \frac{Q^2}{2C}$

(2)  $U_E + U_B = \frac{Q^2}{2C} = \text{constant}$

(3)  $U_E = (U_E)_{\max}$  when  $U_B = 0$ ;  $U_B = (U_B)_{\max}$  when  $U_E = 0$

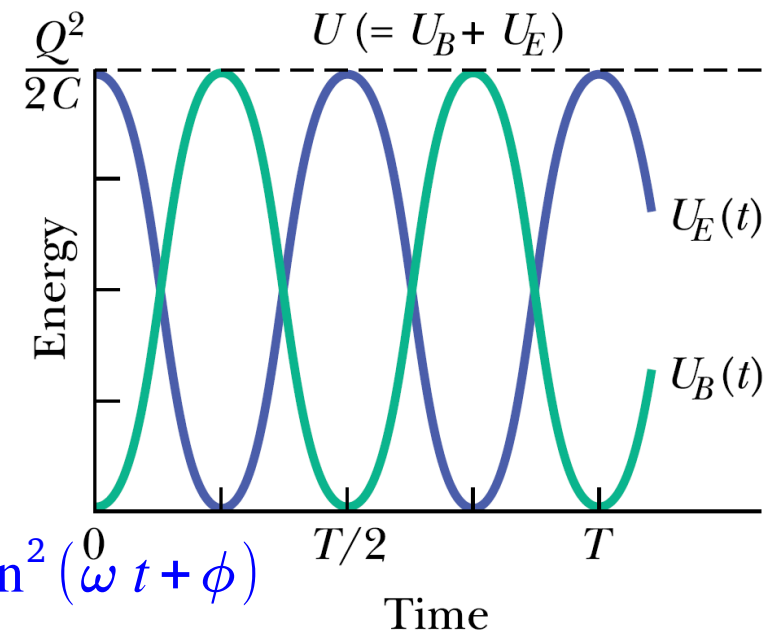

problem 31-1

## Damped Oscillations in an *RLC* Circuit

● A circuit containing resistance, inductance, and capacitance is called an *RLC circuit*. We shall here discuss only *series RLC circuits*

● With a resistance present, the total EM energy of the circuit is no longer constant; it decreases with time as energy is transferred to thermal energy in the resistance.

● Because of this loss of energy, the oscillations of charge, current, and potential difference decrease in amplitude, and the oscillations are *damped*.


● The rate of energy transferred to thermal energy:  $\frac{dU}{dt} = -i^2 R$

$$\Rightarrow \frac{d}{dt} \left( \frac{L i^2}{2} + \frac{q^2}{2C} \right) = L i \frac{di}{dt} + \frac{q}{C} \frac{dq}{dt} = -i^2 R \Rightarrow L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = 0 \quad \text{RLC circuit}$$

$$\Rightarrow q = Q e^{-Rt/2L} \cos(\omega' t + \phi) \quad \Leftarrow \quad \omega' = \sqrt{\omega^2 - (R/2L)^2} \leq \omega \quad \Leftarrow \quad \omega = 1/\sqrt{LC}$$

● The electrical energy:  $U_E = \frac{q^2}{2C} = \frac{Q^2}{2C} e^{-Rt/L} \cos^2(\omega' t + \phi) \Rightarrow U = \frac{Q^2}{2C} e^{-Rt/L}$

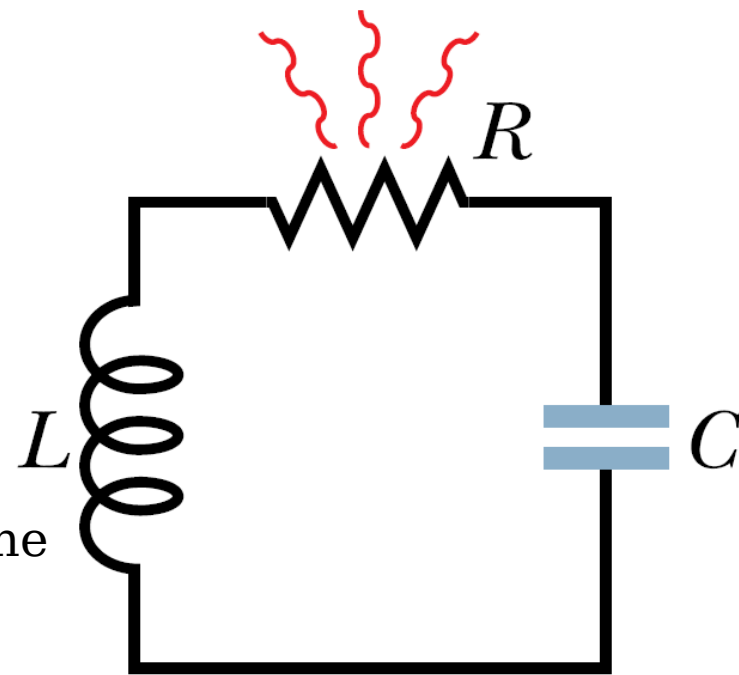
the magnetic energy:  $U_B = \frac{L i^2}{2} = \frac{Q^2}{2C} e^{-Rt/L} \sin^2(\omega' t + \phi)$


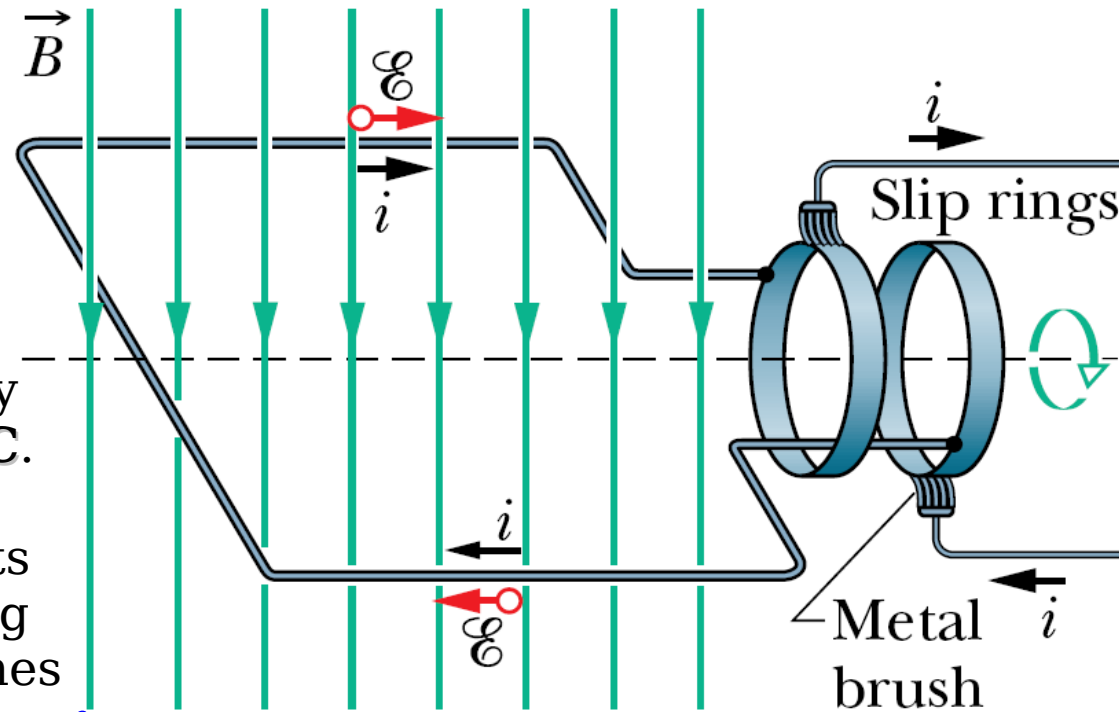
## Alternating Current

● If the energy is supplied via oscillating emfs and currents, the current is said to be an **alternating current**, or **AC** for short. The nonoscillating current from a battery is said to be a **direct current**, or **DC**.

● These oscillating emfs and currents vary sinusoidally with time, reversing direction (in North America) 120 times per second and thus having frequency  $f = 60 \text{ Hz}$ .



● The advantage of alternating current: *As the current alternates, so does the magnetic field that surrounds the conductor.* This makes possible the use of Faraday's law of induction.


● In a generator:  $\mathcal{E} = \mathcal{E}_m \sin \omega_d t$ ,  $i = I \sin (\omega_d t - \phi)$  where  $\omega_d$  is called the **driving angular frequency**.

● The current may not be in phase with the emf.

● The **driving frequency**  $f_d = \frac{\omega_d}{2\pi}$
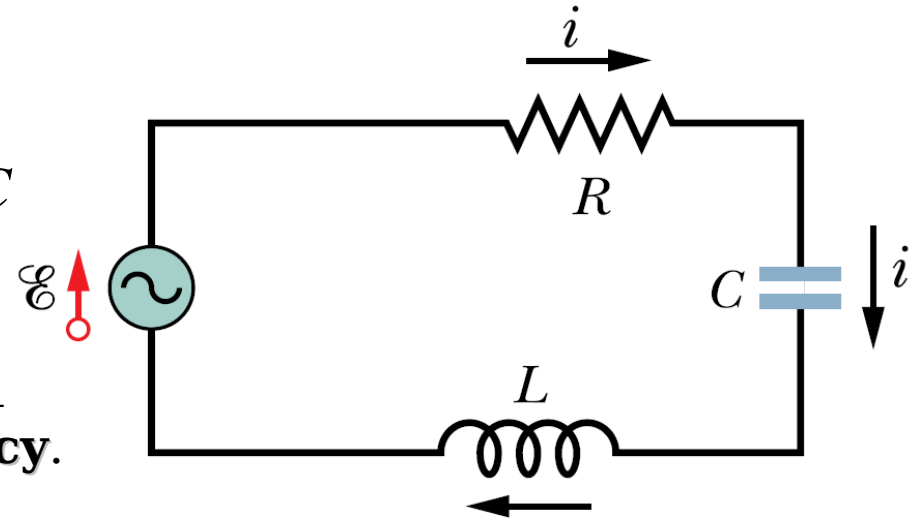
## Forced Oscillations

● An undamped  $LC$  circuits or a damped  $RLC$  circuits (with small enough  $R$ ) without any external emf are said to be *free oscillations*, and the angular frequency  $\omega = 1/\sqrt{LC}$  is said to be the circuit's **natural angular frequency**.



● When the external alternating emf is connected to an  $RLC$  circuit, the oscillations of charge, potential difference, and current are said to be *driven oscillations* or *forced oscillations*., with the driving angular frequency  $\omega_d$ :

Whatever the natural angular frequency  $\omega$  of a circuit may be, forced oscillations of charge, current, and potential difference in the circuit always occur at the driving angular frequency  $\omega_d$ .


## Three Simple Circuits

### A Resistive Load

● By the loop rule:  $\mathcal{E} - v_R = 0 \Rightarrow v_R = \mathcal{E}_m \sin \omega_d t$


$$\Rightarrow v_R = V_R \sin \omega_d t \Leftrightarrow V_R = \mathcal{E}_m \Rightarrow i_R = \frac{v_R}{R} = \frac{V_R}{R} \sin \omega_d t$$
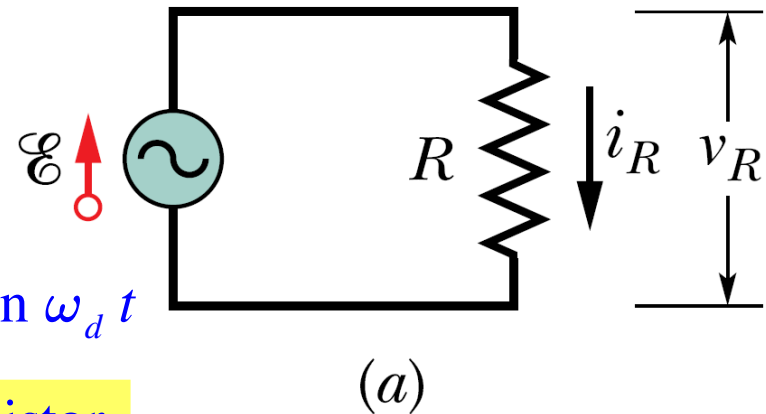
$$i_R = I_R \sin(\omega_d t - \phi) \Rightarrow \phi = 0, \quad V_R = I_R R \text{ resistor}$$




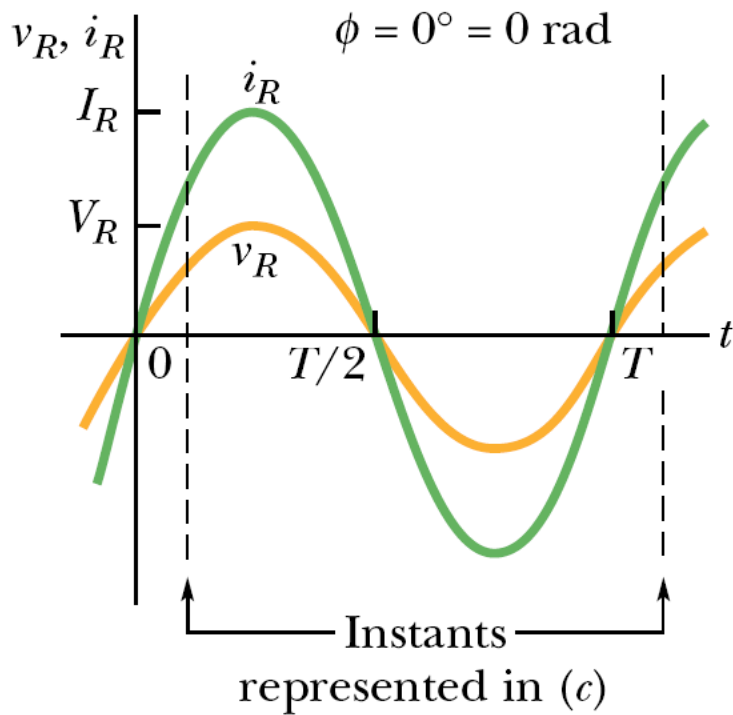●  $v_R$  and  $i_R$  are *in phase*, which means that their corresponding maxima (and minima) occur at the same times.





(b)

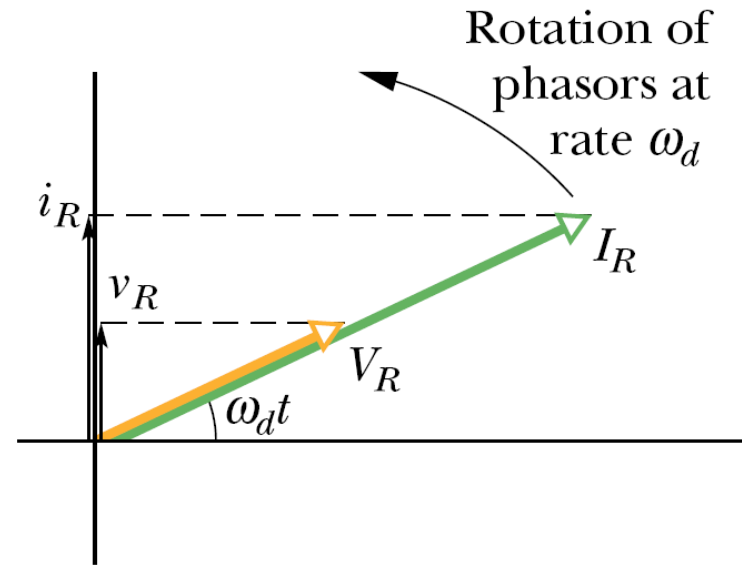

(c) problem 31-3

## A Capacitive Load

- The potential difference across the capacitor

$$v_C = V_C \sin \omega_d t \Rightarrow q_C = C v_C = C V_C \sin \omega_d t$$


- The current:  $i_C = \frac{d q_C}{d t} = \omega_d C V_C \cos \omega_d t$



- Capacitive reactance:**  $X_C = \frac{1}{\omega_d C}$  capacitive reactance

- The SI unit of  $X_C$  is the *ohm*, just as for resistance  $R$ .

- $\cos \omega_d t = \sin \left( \omega_d t + \frac{\pi}{2} \right) \Rightarrow i_C = I_C \sin (\omega_d t - \phi) = \frac{V_C}{X_C} \sin \left( \omega_d t + \frac{\pi}{2} \right)$

$$\Rightarrow V_C = I_C X_C \text{ capacitor} \Leftarrow \text{true for any capacitance in any circuit}$$

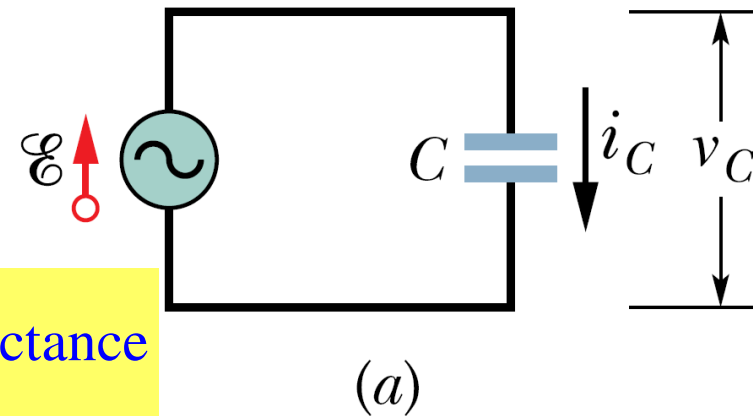

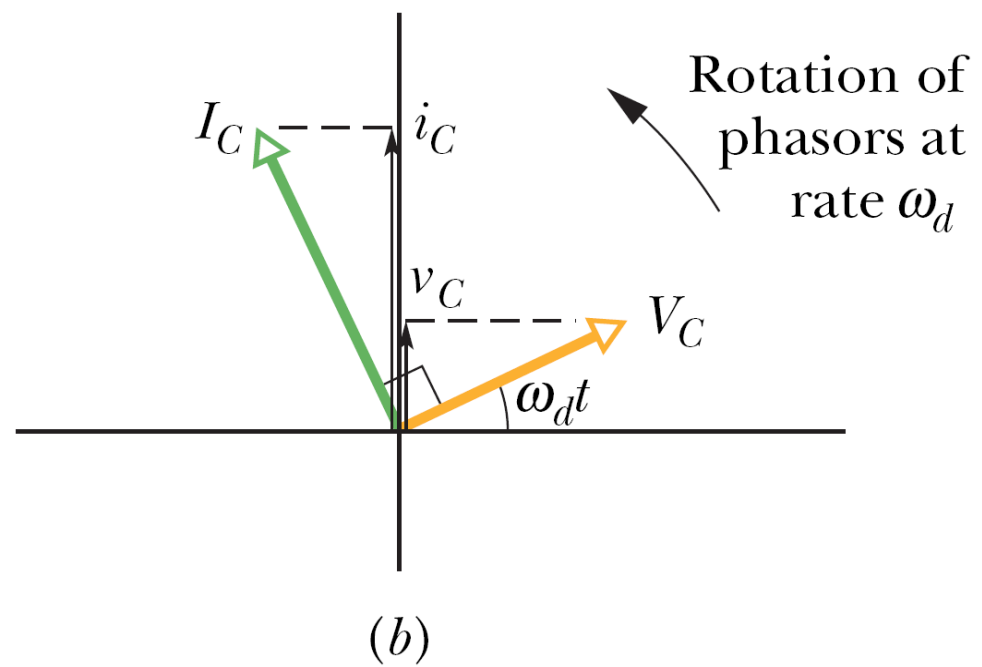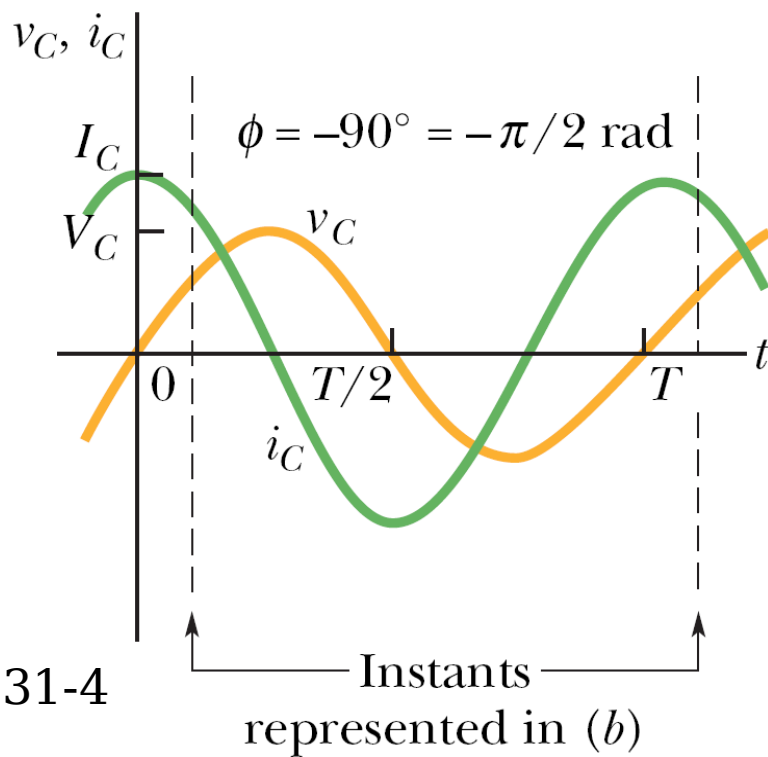

Problem 31-4

Instantants represented in (b)

### An Inductive Load (a)

- The potential difference across the inductance

$$v_L = V_L \sin \omega_d t = L \frac{d i_L}{d t} \Rightarrow \frac{d i_L}{d t} = \frac{V_L}{L} \sin \omega_d t$$


$$i_L = \int d i_L = \frac{V_L}{L} \int \sin \omega_d t d t = -\frac{V_L}{\omega_d L} \cos \omega_d t$$

- Inductive reactance:**  $X_L = \omega_d L$  inductive reactance


- The SI unit of  $X_L$  is the *ohm*, just as for  $X_C$  and for  $R$ .

$$-\cos \omega_d t = \sin \left( \omega_d t - \frac{\pi}{2} \right) \Rightarrow i_L = I_L \sin \left( \omega_d t - \phi \right) = \frac{V_L}{X_L} \sin \left( \omega_d t - \frac{\pi}{2} \right)$$

$$\Rightarrow V_L = I_L X_L \text{ inductor} \Leftarrow \text{true for any inductance in any circuit}$$

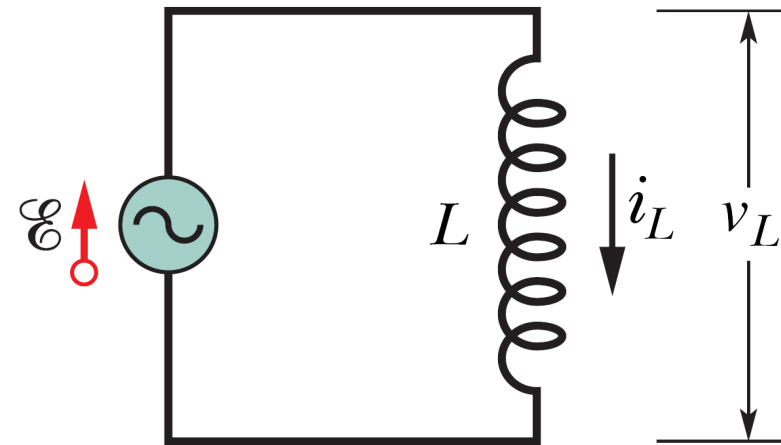

Problem 31-5

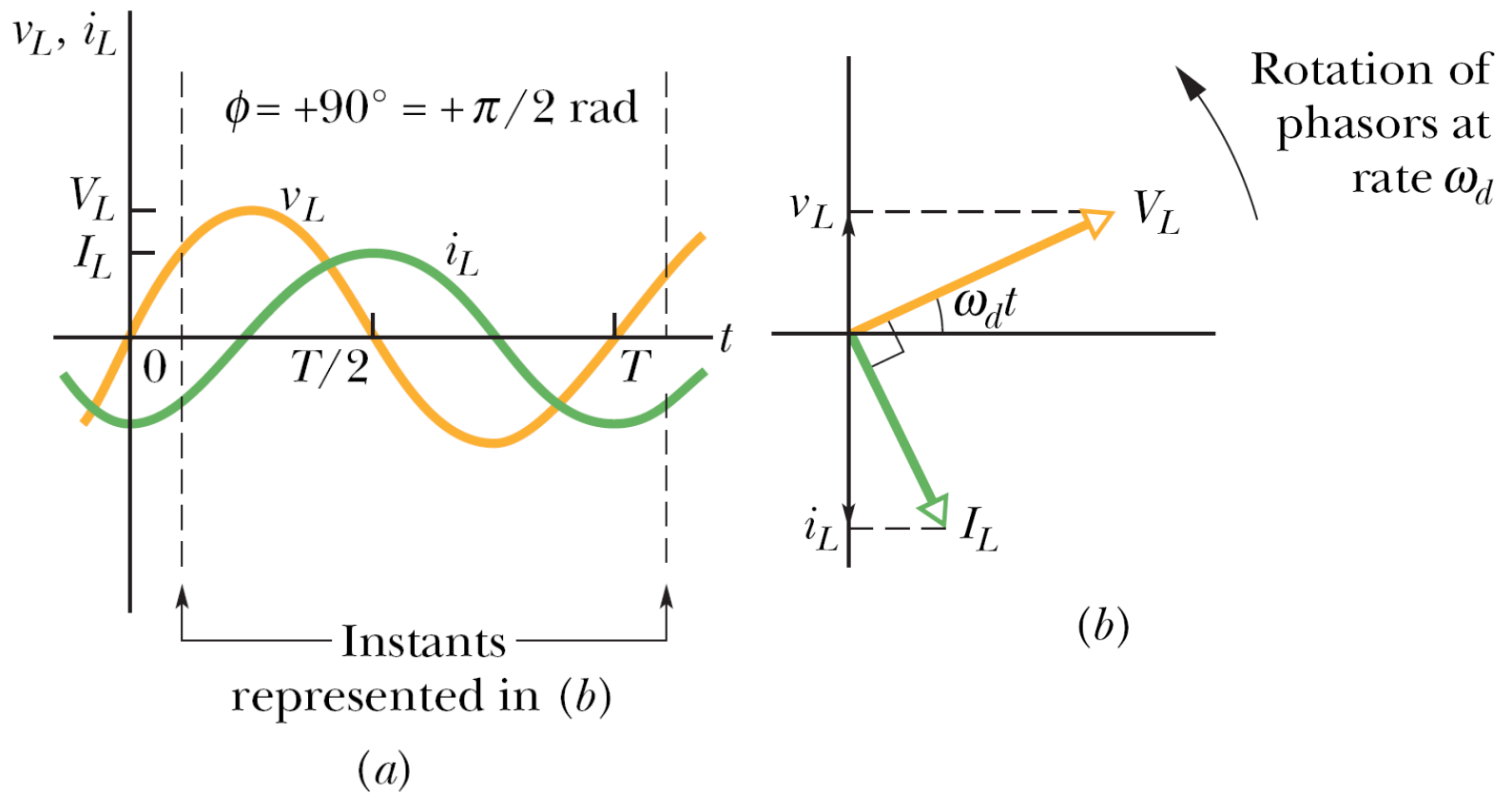


### Phase and Amplitude Relations for Alternating Currents and Voltages

Circuit Element	Symbol	Resistance or Reactance	Phase of the Current	Phase Constant (or Angle) $\phi$	Amplitude Relation
Resistor	$R$	$R$	In phase with $v_R$	0	$V_R = I_R R$
Capacitor	$C$	$X_C = \frac{1}{\omega_d C}$	Leads $v_C$ by $\frac{\pi}{2}$	$-\frac{\pi}{2}$	$V_C = I_C X_C$
Inductor	$L$	$X_L = \omega_d L$	Lags $v_L$ by $\frac{\pi}{2}$	$\frac{\pi}{2}$	$V_L = I_L X_L$
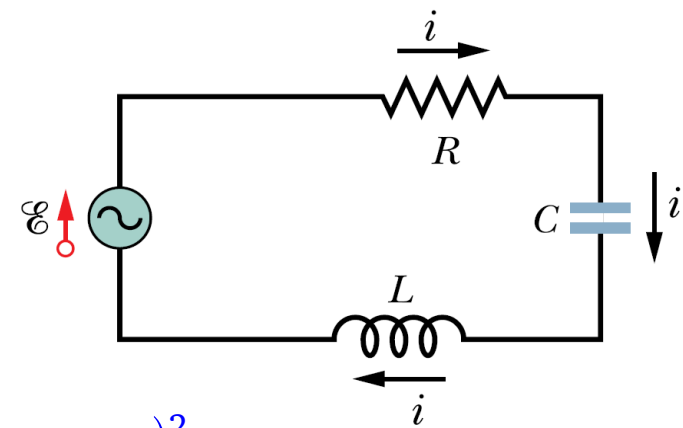
## The Series *RLC* Circuit

- Apply a *RLC* circuit the alternating emf

$$\mathcal{E} = \mathcal{E}_m \sin \omega_d t \quad \text{applied emf} \Rightarrow i = I \sin(\omega_d t - \phi)$$



## The Current Amplitude


- For the loop rule:  $\mathcal{E} = v_R + v_C + v_L \Rightarrow \mathcal{E}_m^2 = V_R^2 + (V_L - V_C)^2$

$$\Rightarrow \mathcal{E}_m^2 = (I R)^2 + (I X_L - I X_C)^2 \Rightarrow I = \frac{\mathcal{E}_m}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{\mathcal{E}_m}{Z} \quad \text{where}$$


$$Z = \sqrt{R^2 + (X_L - X_C)^2} \quad \text{impedance}$$

$$\Rightarrow I = \frac{\mathcal{E}_m}{\sqrt{R^2 + [\omega_d L - 1/(\omega_d C)]^2}} \quad \text{current amplitude}$$

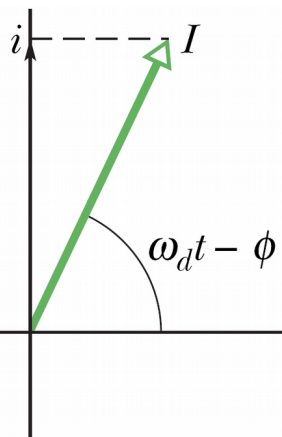
- The value of  $I$  depends on the difference between  $\omega_d L$  and  $1/\omega_d C$  or, equivalently, the difference between  $X_L$  and  $X_C$ .




(a)

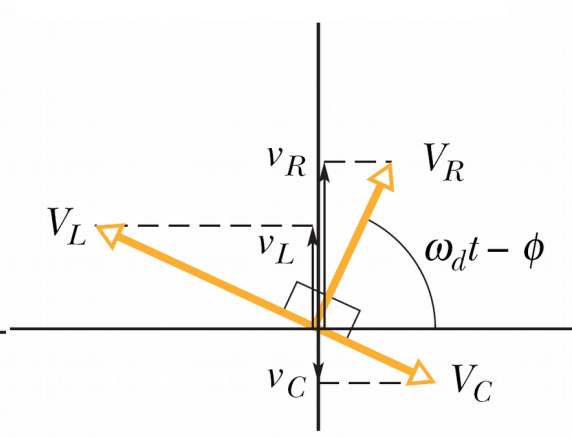

(b)

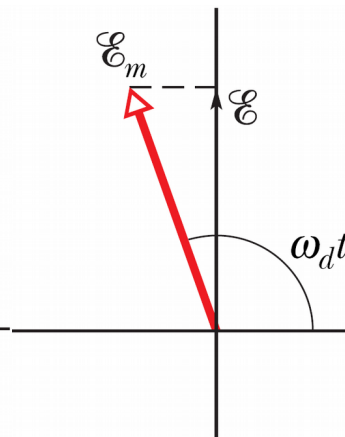

(c)

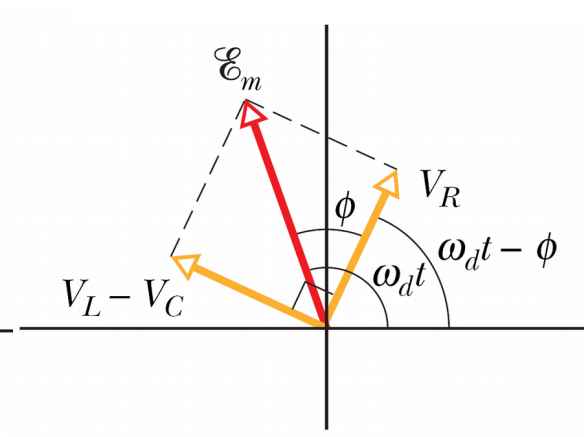

(d)

$$\mathcal{E} = \mathcal{E}_m \sin \omega_d t \Rightarrow i = I \sin (\omega_d t - \phi)$$

$$v_R = i R = V_R \sin (\omega_d t - \phi) \quad V_R = I R$$

$$\Rightarrow v_C = -V_C \cos (\omega_d t - \phi) \Leftarrow V_C = I X_C \Rightarrow \text{Define } V_X = V_L - V_C$$

$$v_L = V_L \cos (\omega_d t - \phi) \quad V_L = I X_L$$

$$\mathcal{E}_m \sin \omega_d t \Leftarrow \mathcal{E} = v_R + v_C + v_L = V_R \sin (\omega_d t - \phi) + V_X \cos (\omega_d t - \phi)$$

$$= (V_R \cos \phi + V_X \sin \phi) \sin \omega_d t + (V_X \cos \phi - V_R \sin \phi) \cos \omega_d t$$

Coefficient comparison gives  $V_R \cos \phi + V_X \sin \phi = \mathcal{E}_m$

$$V_X \cos \phi - V_R \sin \phi = 0$$

$$\Rightarrow \tan \phi = \frac{V_X}{V_R} = \frac{V_L - V_C}{V_R} = \frac{X_L - X_C}{R}$$


$$V_R = \mathcal{E}_m \cos \phi, \quad V_X = \mathcal{E}_m \sin \phi \Rightarrow \mathcal{E}_m^2 = V_R^2 + V_X^2 = V_R^2 + (V_L - V_C)^2$$

- The current that we have been describing in this section is the *steady-state current* that occurs after the alternating emf has been applied for some time.

- When the emf is first applied to a circuit, a brief *transient current* occurs. Its duration is determined by the time constants  $\tau_L=L/R$  and  $\tau_C=RC$  as the inductive and capacitive elements “turn on.”
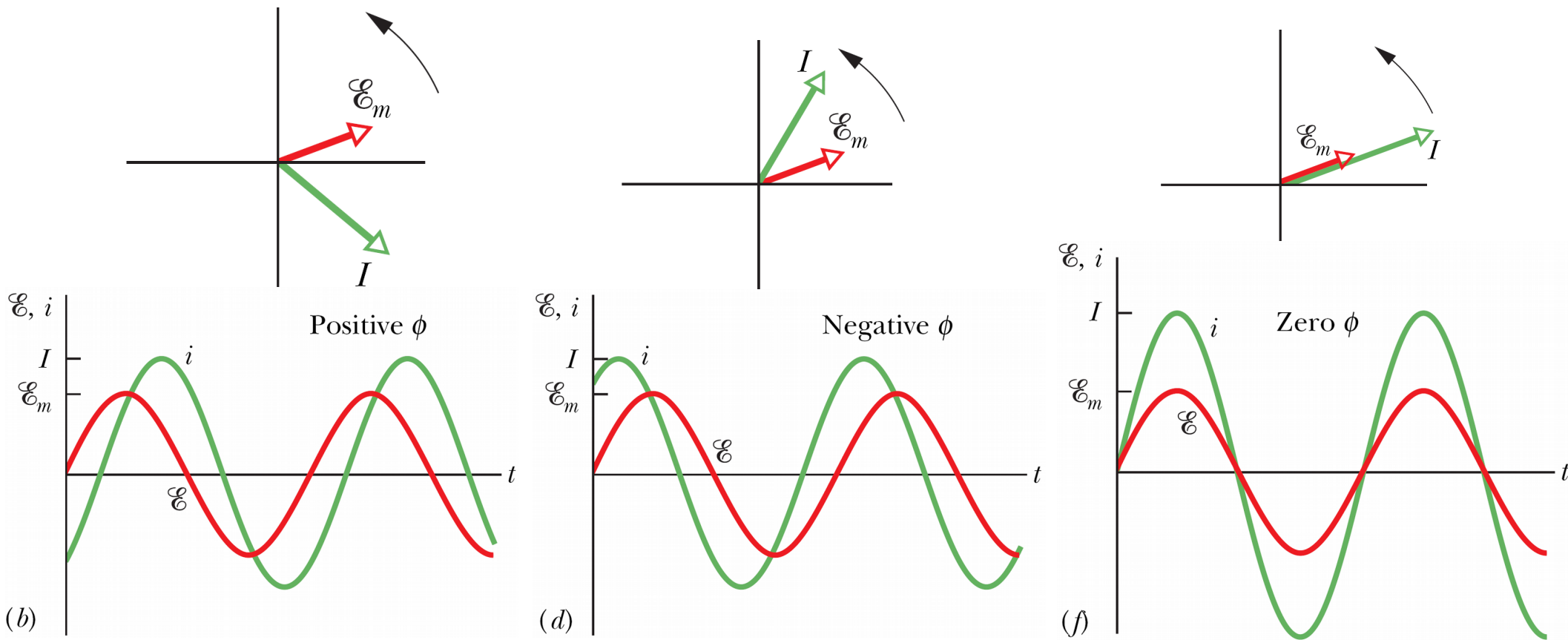
### The Phase Constant

- From the plot:  $\tan \phi = \frac{V_L - V_C}{V_R} = \frac{I X_L - I X_C}{I R} \Rightarrow \tan \phi = \frac{X_L - X_C}{R}$  phase constant



- 3 different results for the phase constant

$X_L > X_C$ : The circuit is said to be *more inductive than capacitive*.

$X_C > X_L$ : The circuit is said to be *more capacitive than inductive*.

$X_C = X_L$ : The circuit is said to be in *resonance*.


- In the *purely inductive circuit*, where  $X_L$  is nonzero and  $X_C = R = 0$ , then  $\phi = \pi/2$  (the greatest value of  $\phi$ ). In the *purely capacitive circuit*, where  $X_C$  is nonzero and  $X_L = R = 0$ , then  $\phi = -\pi/2$  (the least value of  $\phi$ ).

## Resonance

- For a given resistance  $R$ , that amplitude is a maximum when the quantity  $\omega_d L - 1/\omega_d C$  in the denominator is 0

$$\omega_d L = \frac{1}{\omega_d C} \Rightarrow \omega_d = \frac{1}{\sqrt{LC}} \quad \text{maximum } I$$

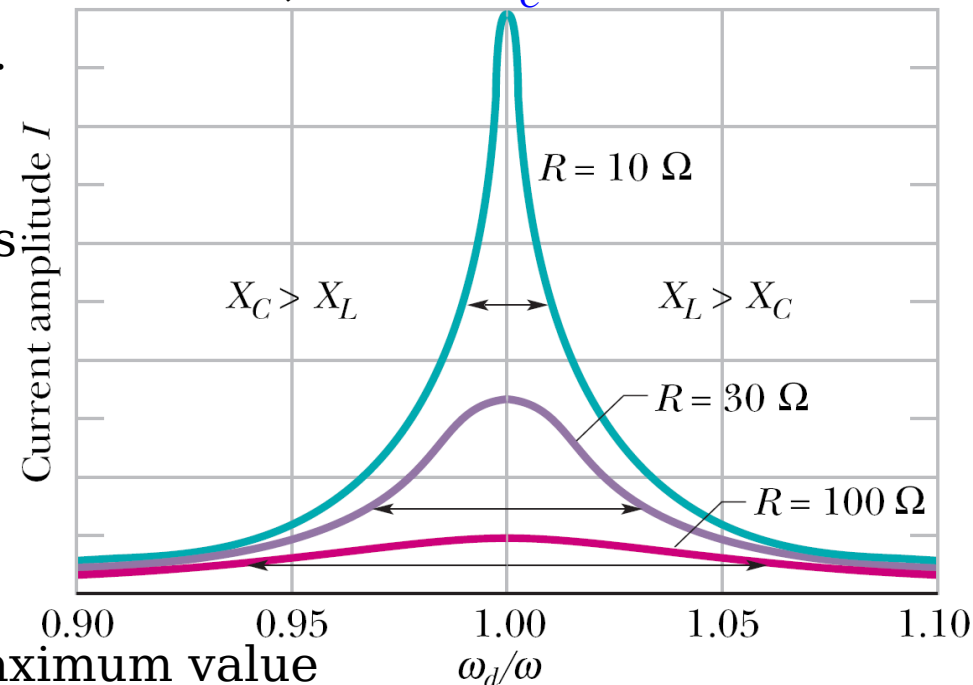- The natural angular frequency  $\omega$  of the  $RLC$  circuit is also equal to  $1/\sqrt{LC}$ , the maximum value of  $I$  occurs when the driving angular frequency matches the natural angular frequency—that is, at resonance.



$$\omega_d = \omega = \frac{1}{\sqrt{LC}} \quad \text{resonance}$$

- The *resonance curves* peak at their maximum current amplitude  $I (= \mathcal{E}_m/R)$  when  $\omega_d = \omega$ , but the maximum value of  $I$  decreases with increasing  $R$ . The curves also increase in width (measuring at half the maximum value of  $I$ ) with increasing  $R$ .
- For small  $\omega_d$ ,  $X_L (= \omega_d L)$  is small and  $X_C (= 1/\omega_d C)$  is large. Thus, the circuit is mainly capacitive and the impedance is dominated by the large  $X_C$ , which keeps the current low.
- As  $\omega_d$  increases,  $X_C$  remains dominant but decreases while  $X_L$  increases. The decrease in  $X_C$  decreases the impedance, allowing the current  $I$  to increase. When the increasing  $X_L$  and the decreasing  $X_C$  reach equal values, the current  $I$  is greatest and the circuit is in resonance, with  $\omega_d = \omega$ .
- As  $\omega_d$  continue to increase, the increasing  $X_L$  becomes more dominant over the decreasing  $X_C$ . The impedance increases because of  $X_L$  and the current decreases.
- In summary: The low-angular-frequency side of a resonance curve is dominated by the capacitor's reactance, the high-angular frequency side is dominated by the inductor's reactance, and resonance occurs in the middle.



## Power in Alternating-Current Circuits

- In steady-state operation the average energy stored in the capacitor and inductor together remains constant. The net transfer of energy is thus from the generator to the resistor, where EM energy is dissipated as thermal energy.

- The instantaneous rate at which energy is dissipated in the resistor


$$P = i^2 R = [I \sin(\omega_d t - \phi)]^2 R = I^2 R \sin^2(\omega_d t - \phi)$$

- The *average* rate at which energy is dissipated

$$P_{\text{avg}} = \frac{1}{T} \int_0^T P \, dt = \frac{I^2 R}{T} \int_0^T \sin^2(\omega_d t - \phi) \, dt = \frac{I^2 R}{2}$$

$$= \left( \frac{I}{\sqrt{2}} \right)^2 R \Rightarrow I_{\text{rms}} \equiv \frac{I}{\sqrt{2}} \quad \text{rms current}$$

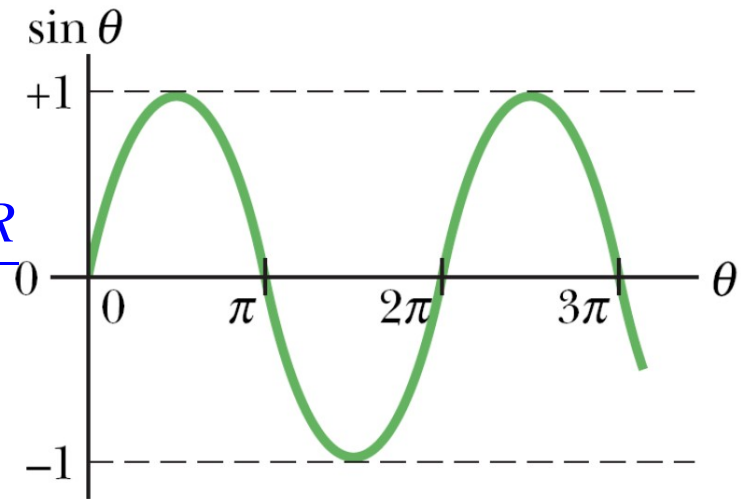
$$\Rightarrow P_{\text{avg}} = I_{\text{rms}}^2 R \quad \text{average power}$$



(a)

- If we switch to the rms current, we can compute the average rate of energy dissipation for alternating-current circuits just as for direct-current circuits.
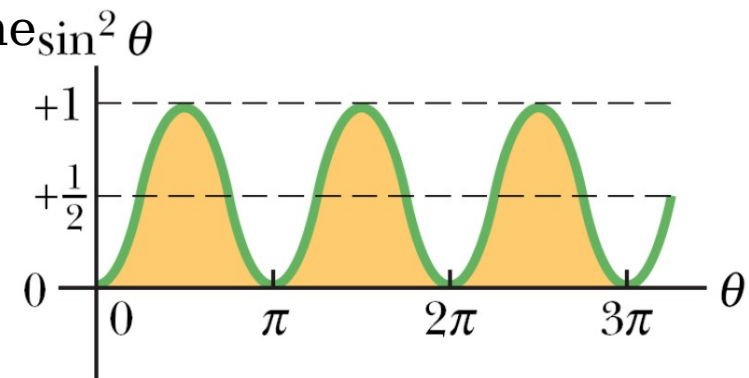
$$\bullet V_{\text{rms}} = \frac{V}{\sqrt{2}}, \quad \mathcal{E}_{\text{rms}} = \frac{\mathcal{E}}{\sqrt{2}} \quad \text{rms voltage; rms emf}$$



(b)

- Alternating-current instruments, such as ammeters and voltmeters, are usually calibrated to read  $I_{\text{rms}}$ ,  $V_{\text{rms}}$ , and  $\mathcal{E}_{\text{rms}}$ .

- Plug an alternating-current voltmeter into a electrical outlet and it reads 120 V, that is an rms voltage. The maximum value of the potential difference at the outlet is  $\sqrt{2} \times (120 \text{ V})$  or 170 V.

- $$I_{\text{rms}} = \frac{\mathcal{E}_{\text{rms}}}{Z} = \frac{\mathcal{E}_{\text{rms}}}{\sqrt{R^2 + (X_L - X_C)^2}} \Rightarrow P_{\text{avg}} = \frac{\mathcal{E}_{\text{rms}}}{Z} I_{\text{rms}} R = \mathcal{E}_{\text{rms}} I_{\text{rms}} \frac{R}{Z}$$

$$\Rightarrow P_{\text{avg}} = \mathcal{E}_{\text{rms}} I_{\text{rms}} \cos \phi \quad \text{average power} \quad \Leftarrow \quad \cos \phi = \frac{V_R}{\mathcal{E}_m} = \frac{I R}{I Z} = \frac{R}{Z} \quad \begin{array}{l} \text{power} \\ \text{factor} \end{array}$$

- The equation is independent of the sign of the phase constant  $\phi \Leftarrow \cos \phi = \cos(-\phi)$ .

- To maximize the rate at which energy is supplied to a resistive load in an *RLC* circuit, we should keep the power factor  $\cos \phi$  as close to 1 as possible  $\Leftarrow \phi = 0$ .

Problem 31-7

# Transformers

## Energy Transmission Requirements

- An ac circuit with only a resistive load, the power factor  $\cos 0=1$ ,  $P_{\text{avg}} = \mathcal{E} I = I V$
- A range of choices of  $I$  and of  $V$  provided only that the product  $IV$  is as required.
- In the transmission of electrical energy from the generating plant to the consumer, we want the lowest practical current (hence the largest practical voltage) to minimize  $I^2R$  losses (often called ohmic losses) in the transmission line.
- Consider a 735 kV line to transmit electrical energy for 1000 km. If the current is 500 A and the power factor  $\sim$  unity. Then

$$P_{\text{avg}}^{\text{supply}} = \mathcal{E} I = (735000 \text{ V})(500 \text{ A}) = 368 \text{ MW}$$

- The resistance of the transmission line is about  $0.22\Omega/\text{km} \Rightarrow R_{\text{total}} = 220 \Omega$   
Energy is dissipated due to that resistance at a rate

$$P_{\text{avg}}^R = I^2 R = (500 \text{ A})^2 (220 \Omega) = 55 \text{ MW} \sim 15 \% \times P_{\text{avg}}^{\text{supply}}$$

- In the other case:  $I' = 2I$ ,  $\mathcal{E}' = \frac{\mathcal{E}}{2} \Rightarrow P_{\text{avg}}^{\text{supply}} = \mathcal{E}' I' = \mathcal{E} I$


$$\Rightarrow P_{\text{avg}}^R = I'^2 R = (1000 \text{ A})^2 (220 \Omega) = 220 \text{ MW} \sim 65 \% \times P_{\text{avg}}^{\text{supply}}$$

- The general energy transmission rule: Transmit at the highest possible voltage and the lowest possible current.
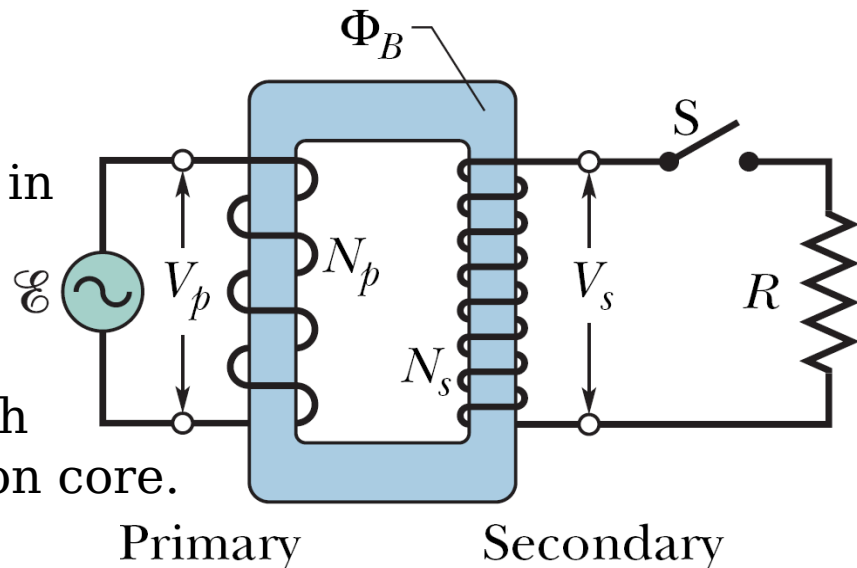
## The Ideal Transformer

● Need a device with which we can raise (for transmission) and lower (for use) the ac voltage in a circuit, keeping the product current voltage essentially constant  $\Rightarrow$  the **transformer**.

● The *ideal transformer* consists of two coils, with different numbers of turns, wound around an iron core.



● The primary winding, of  $N_p$  turns, is connected to an AC generator whose emf is

$$\mathcal{E} = \mathcal{E}_m \sin \omega t$$

● The secondary winding, of  $N_s$  turns, is connected to load resistance  $R$ .

● The primary current, the *magnetizing current*  $I_{\text{mag}}$ , lags the primary voltage  $V_p$  by  $90^\circ$  (no power is delivered). The sinusoidally changing primary current  $I_{\text{mag}}$  produces a sinusoidally changing magnetic flux  $\Phi_B$  in the iron core.

● The core strengthens the flux and to bring it through the secondary winding.

● Because  $\Phi_B$  varies, it induces an emf  $\mathcal{E}_{\text{turn}}$  ( $d\Phi_B/dt$ ) in each turn of the secondary. the emf per turn  $\mathcal{E}_{\text{turn}}$  is the same in the primary and the secondary

$$\mathcal{E}_{\text{turn}} = \frac{V_p}{N_p} = \frac{V_s}{N_s} \Rightarrow V_s = V_p \frac{N_s}{N_p} \quad \text{transformation of voltage}$$

- $N_s > N_p$ : *step-up transformer* because  $V_s > V_p$  ;  
 $N_s < N_p$ : *step-down transformer* because  $V_s < V_p$  .

● Connect the secondary to the resistive load  $R$ , now energy is transferred from the generator:

- 1 An AC  $I_s$  appears in a secondary circuit, with corresponding energy dissipation rate  $I_s^2 R (= V_s^2 / R)$  in the resistive load.
- 2  $I_s$  produces its own alternating magnetic flux in the iron core, and this flux induces an opposing emf in the primary windings.
- 3  $V_p$  of the primary cannot change in response to this opposing emf because it must always be equal to the emf that is provided by the generator.
- 4 To maintain  $V_p$ , the generator now produces (in addition to  $I_{\text{mag}}$ ) an AC  $I_p$  in the primary circuit; the emf induced by  $I_p$  in the primary will exactly cancel the emf induced there by  $I_s$ . Because the phase constant of  $I_p$  is not  $90^\circ$  like that of  $I_{\text{mag}}$ , this current  $I_p$  can transfer energy to the primary.

- Assume no energy is lost, conservation of energy requires that

$$I_p V_p = I_s V_s \Rightarrow I_s = I_p \frac{N_p}{N_s} \quad \text{transformation of currents}$$

$$\Rightarrow I_p = I_s \frac{N_s}{N_p} = \frac{N_s}{N_p} \frac{V_s}{R} = \left( \frac{N_s}{N_p} \right)^2 \frac{V_p}{R} \equiv \frac{V_p}{R_{\text{eq}}} \Rightarrow R_{\text{eq}} = \left( \frac{N_p}{N_s} \right)^2 R$$


## Impedance Matching

- For maximum transfer of energy from an emf device to a load, the impedance of the emf device must equal the impedance of the load. We can match the impedances of the two devices by coupling them through a transformer that has a suitable turns ratio.

## Solar Activity and Power-Grid Systems

problem 31-8

Selected problems: 22, 26, 36,50, 58

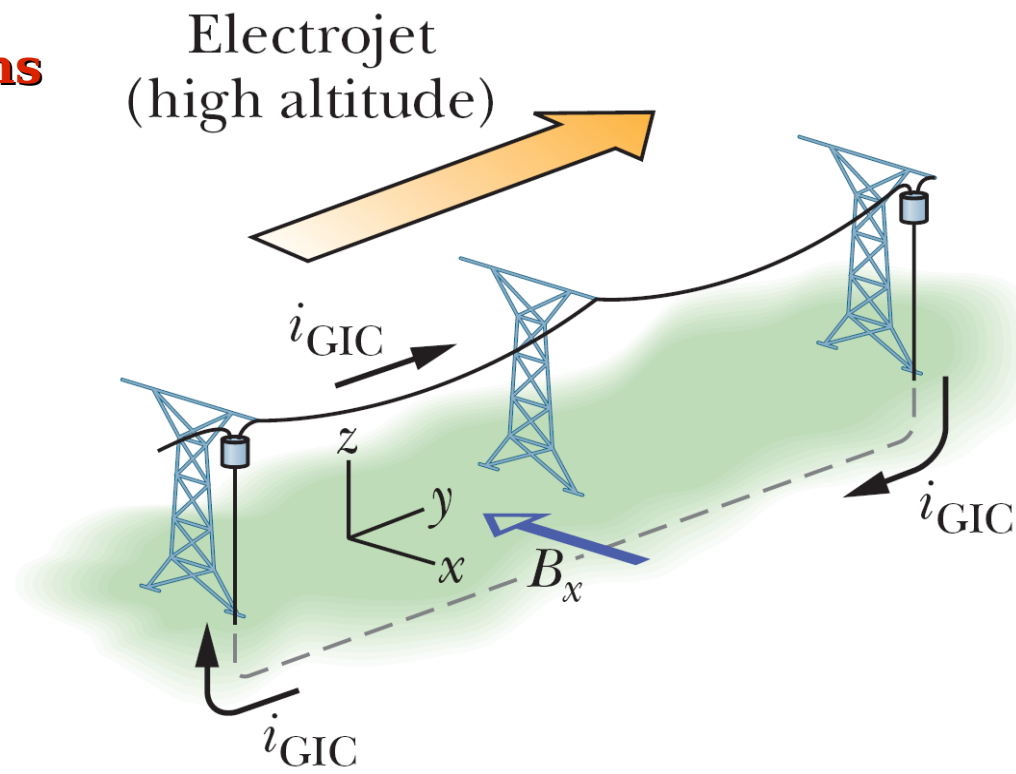

# Impedance Matching and Maximum Power Transfer

$$R_S \neq 0 \Rightarrow I = \frac{V_S}{R_S + R_L}$$

$$\Rightarrow P_L \equiv I^2 R_L = \frac{V_S^2 R_L}{(R_S + R_L)^2}$$

$$\text{To find } P_{L, \max} \Rightarrow \frac{d P_L}{d R_L} = 0$$

$$\Rightarrow R_L = R_S \Rightarrow P_{L, \max} = \frac{V_S^2}{4 R_S}$$

